

Roll No. 22EBAC4033

Total Page No. : 3

31N0402 /

31N0402

**B.TECH. III SEM MAIN/BACK (NEW SCHEME)
ACADEMIC SESSION 2023-24**

(Artificial Intelligence And Data Science)

III And Other Branches

3AD4-02 - Digital Electronics

Common to CS, IT, AI, DS, MC, CM, CD, CA, AD, AM, CY, IO

Time : 3 Hours]

[Max. Marks : 70

[Min. Passing Marks :

Instructions to Candidates :

Part-A : Short Answer Type Questions (up to 25 words) $10 \times 2 = 20$ marks. All 10 questions are compulsory.

Part-B : Analytical/Problem Solving questions $5 \times 4 = 20$ marks. Candidates have to answer 5 questions out of 7.

Part-C : Descriptive/Analytical/Problem Solving questions 3×10 marks = 30 marks. Candidates have to answer 3 questions out of 5.

Schematic diagrams must be shown wherever necessary. Any data you feel missing may suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Use of the following supporting materials is permitted during examination.
(Mentioned in form no. 205).

1_NIL_____

2_NIL_____

F-027

(1)

P.T.O.

Part-A

10×2=20

- Q. 1. Find the 1's complement of the following binary numbers : [2]
- (a) (11100)₂
- (b) (1101)₂
- Q. 2. Realise the expression $Y = \overline{A}\overline{B} + \overline{A}B$ using only NAND gates. [2]
- Q. 3. Draw the block diagram of a full subtractor. [2]
- Q. 4. What are shift registers ? [2]
- Q. 5. What is a logic family ? [2]
- Q. 6. Define fan-in and fan-out. [2]
- Q. 7. What is the difference between Asynchronous and synchronous counters ? [2]
- Q. 8. How does a decoder differ from an encoder ? [2]
- Q. 9. Explain the difference between SOP and POS forms. [2]
- Q. 10. Express the number (137)₁₀ in BCD and binary. [2]

Part-B

5×4=20

- Q. 1. What is the necessary condition for a weighted code to be self-complementing ? [4]
- Give two examples of weighted codes.
- Q. 2. Simplify the following equation using the K-mapping procedure : [4]
- $$X = \overline{A}\overline{B}\overline{D} + A\overline{C}\overline{D} + \overline{A}B\overline{C} + AB\overline{C}D + A\overline{B}C\overline{D}$$
- Q. 3. Convert the following number into the respective index given : [4]
- (a) $(89)_{10} = ()_2 = ()_{16}$
- (b) $(1011.101101)_2 = ()_8 = ()_{10}$
- Q. 4. Explain in detail the working of Finite state machines. [4]

- Q. 5. Prove the following identities using Boolean algebra and DeMorgan's theorems : [4]

(a) $\overline{AB + BC + CA} = \overline{A}\overline{B} + \overline{B}\overline{C} + \overline{C}\overline{A}$

(b) $AB + \overline{AC} + A\overline{B}C(AB + C) = 1$

- Q. 6. Describe a simple four-line multiplexer with a Logic Diagram. [4]

- Q. 7. Describe the advantages and disadvantages of ECL. Why is ECL faster than TTL ? [4]

Part-C

3×10=30

- Q. 1. Draw the logic circuit for the following equations. Simplify the equations and draw the simplified logic circuits : [10]

(a) $V = AC + ACD + CD =$

(b) $W = (BCD + C)CD$

(c) $X = (B + D)(A + C) + ABD$

(d) $Y = AB + BC + ABC$

(e) $Z = ABC + CD + CDE$

- Q. 2. Simplify the Boolean function $F(W, X, Y, Z) = \sum m(1, 3, 7, 11, 15)$ and the don't-care conditions $d(W, X, Y, Z) = \sum m(0, 2, 5)$. [10]
- Q. 3. Discuss the detailed procedure for the analysis of combinational circuits. [10]
- Q. 4. Explain the noise margin and figure of merit of a logic family. List the differences between the TTL logic family and the MOS family. [10]
- Q. 5. Explain the different types of flip flops along with their truth table. [10]
